

CSD

2023/2024 – 1º Semestre

Relatório Trabalho 1 - Relógio de Parede

Identificação

Turno: P1

Data: 18 / 11 /2023

Aluno: Guilherme Concha

Número: 60143

Aluno: Pedro Peres

Número: 60495

Aluno: António Alves

Número: 58339

Índice

Solução Implementada.....	3
Análise da solução.....	4
1. Máquina de Estados de Edição.....	4
2. Máquina de Estados de Modo.....	4
Implementação.....	5
Resultados.....	6
1. Teste do Relógio.....	6
2. Teste do Alarme.....	6
3. Teste do Temporizador.....	7
4. Teste do Cronómetro.....	7
5. Teste da Máquina de Estados de Edição.....	7
6. Teste da Máquina de Estados de Modo.....	8
7. Teste do Principal.....	8
Anexos.....	9
1. Relógio.....	9
2. Alarm.....	10
3. Timer.....	12
4. Stopwatch.....	14
5. Conversor do Display.....	15
6. Máquina de Estados do Modo.....	16
7. Máquina de Estados da Edição.....	17
8. Debouncer.....	20

Solução Implementada

Este trabalho tem como objetivo a implementação de um relógio de parede através da ferramenta Xilinx ISE e com um FPGA.


A solução implementada para este problema foi um **Relógio** com a funcionalidade de podermos acertar horas, minutos e segundos. Existe um **interruptor de edição**¹ que faz parar o relógio para o fazermos. Para essa edição existe um **botão**¹² para selecionarmos Horas, Minutos ou Segundos e outro **botão**¹¹ para incrementar o que selecionamos através do botão mencionado anteriormente. Existe também um **interruptor**² para mostrar no **Display**³ do FPGA HH:MM e MM:SS.

Tem uma funcionalidade de **Alarme** que acende um **LED**⁴ quando está a “tocar”. Possui um **interruptor**⁵ de edição do alarme como o do relógio.

Tem também uma funcionalidade de **Temporizador** que possui um **LED**⁶ quando está **ativo**. Possui um **interruptor**⁷ que quando está ativo podemos meter o tempo que queremos que seja contado, e quando for desativado o tempo começa a contar até chegar a **zero**.

Por fim tem uma funcionalidade de **Cronómetro**, sendo o mais simples possível com um **interruptor**⁸ que quando está ativo o tempo encontra-se parado e quando está desativado o tempo está a contar. Possui um **botão de reset**⁸ para este voltar a zero.

 Para a Seleção de modo temos um **botão**⁹, e para reset global temos um **botão**¹⁰ também.




Análise da solução

Para a realização da nossa solução necessitamos de desenvolver duas máquinas de estados, para além da programação dos componentes Relógio, Alarme, Temporizador e Cronómetro.

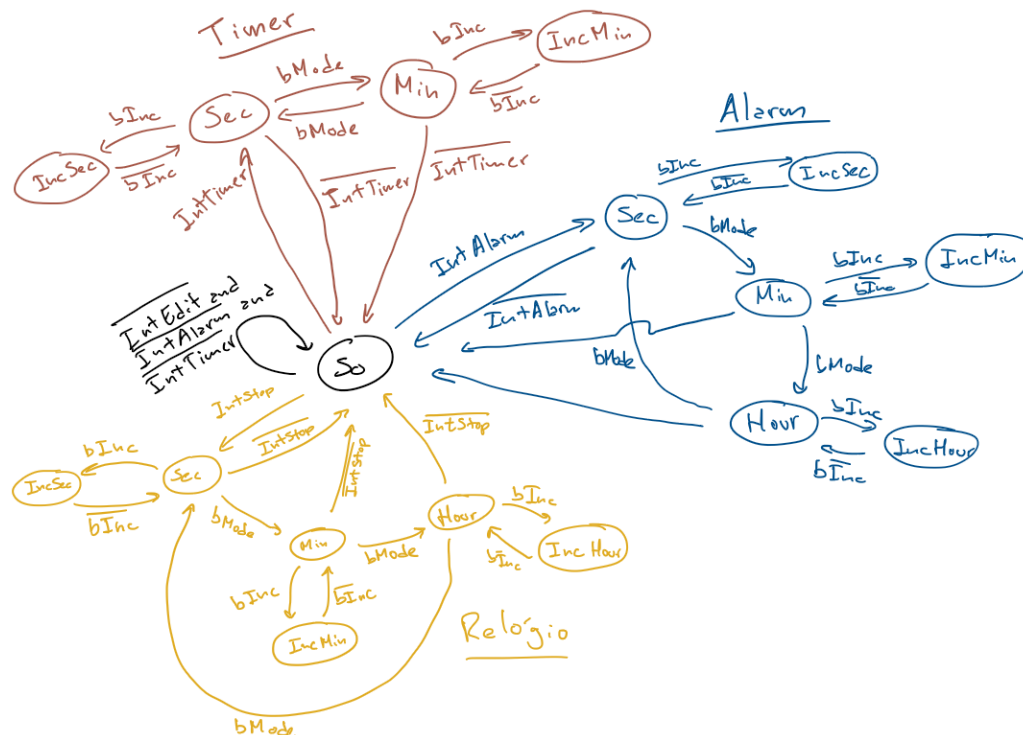
1. Máquina de Estados de Edição

Esta máquina de estados permite-nos enviar para cada um dos componentes um signal para ser incrementado o valor de Segundos / Minutos / Horas.



 
2. Máquina de Estados de Modo

Esta máquina de estados permite ao Display saber o que tem que mostrar ao Utilizador. Através do buttonTypeMode é alternado o estado Relógio, Alarme, Temporizador e Cronómetro, sendo que em cada estado uma variável tem um valor diferente correspondente a cada um dos modos.



Implementação

 O projeto é composto por um core IP, um Debouncer e um Display.



No **core IP**, ou “principal” (nome atribuído no projeto) é responsável por tudo o que aparece no Display, sendo preciso o processamento dividido por vários componentes:

- Relógio*;
- Alarm*;
- Timer*;
- StopWatch*;
- Conversor do Display*;
- Máquina de Estados do Modo*;
- Máquina de Estados da Edição*.

O **Debouncer*** tem o objetivo de retirar o “lag” dos botões do FPGA, ou seja, quando clicamos, apenas ser contado o click durante um clock.


No **Display** aparece o que o User quer, sendo o relógio, alarme, temporizador ou cronómetro.

*Os códigos de cada um dos componentes encontra-se em anexo.

```
entity principal is
    Port ( reset : in std_logic;
          clk : in std_logic;
          algarismo : out std_logic_vector(7 downto 0);
          switch1 : in std_logic;
          switchEDIT : in std_logic;
          switchTIMER : in std_logic;
          switchALARM : in std_logic;
          switchStopWatch : in std_logic;
          buttonMODE : in std_logic;
          buttonTYPEMODE : in std_logic;
          buttonINC : in std_logic;
          LED_Alarm : out std_logic;
          LED_Timer : out std_logic;
          an3 : out std_logic;
          an2 : out std_logic;
          an1 : out std_logic;
          an0 : out std_logic);
end principal;
```

Resultados

1. Teste do Relógio

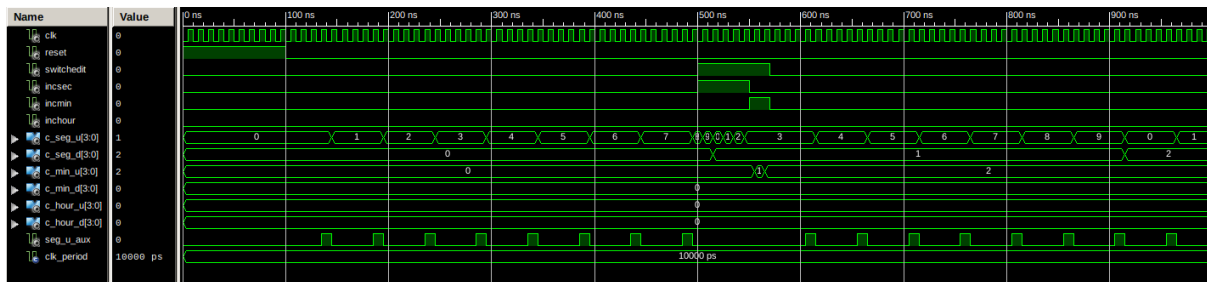


Através desta simulação podemos ver o comportamento do relógio. Temos a variável seg_u_aux que nos diz se o número de clocks que passou representa 1 segundo para o contador dos segundos incrementar.

Em 500 ns na simulação, liguei o interruptor de edição, o relógio parou como era suposto, e incrementei 5 vezes o número de segundos e 2 vezes o número de minutos.

Após ter desligado o interruptor de edição ele continuou a contar a partir do tempo que eu inseri.


2. Teste do Alarme

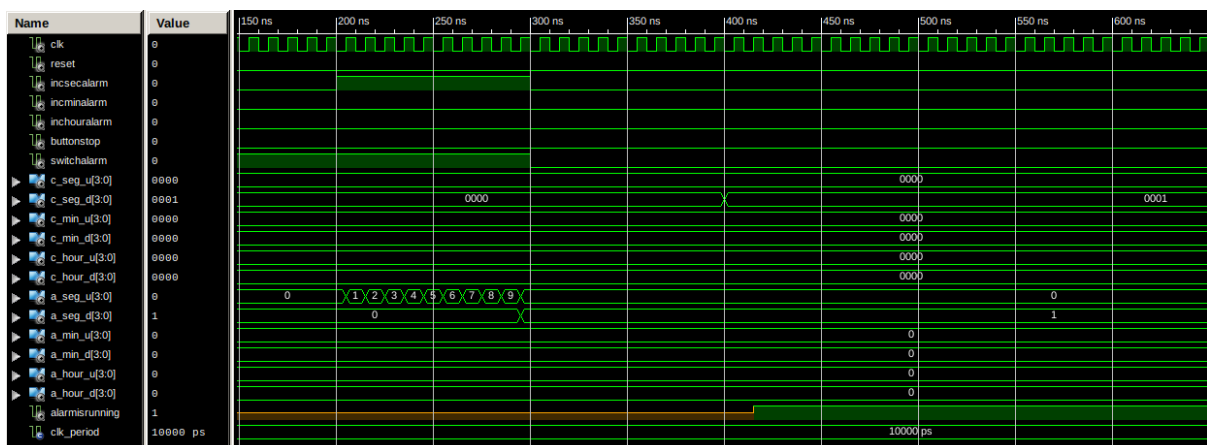

Através desta simulação podemos ver o comportamento do alarme. Começando por ativar o interruptor de edição (switchAlarm), incremento os segundos 10 vezes.

Em 400 ns na simulação, coloquei o tempo do relógio igual ao tempo do alarme e podemos ver que a variável "alarmIsRunning" ficou a 1.


3. Teste do Temporizador

 

Através desta simulação podemos ver o comportamento do temporizador. Começo por ativar o interruptor de edição (switchTimer), para incrementar os Minutos e os Segundos 10 vezes, obtendo 10:10.

Em 300 ns na simulação desativo o interruptor e o tempo começa a decrementar como podemos ver.

4. Teste do Cronómetro

 

Através desta simulação podemos ver o comportamento do cronómetro. O tempo começa logo a contar, e em 500 ns quando ativo o interruptor o mesmo para de incrementar.

Desligando o interruptor o tempo volta a ser incrementado e em 670 ns clico no reset e o tempo volta a 0, começando a contar de 0.


5. Teste da Máquina de Estados de Edição



Através desta simulação podemos ver o comportamento da Máquina de Estados de Edição. O botão de incremento faz uma variável ficar a 1 consoante o modo em que se encontra, e o botão de modo faz alternar entre modos, seg/min/hour.


Entre 200 ns e 300 ns testámos a parte de acerto do relógio. Entre 330 ns e 430 ns testámos a parte de acerto do alarme. E por fim entre 460 ns e 520 ns testámos a parte de acerto do temporizador.

6. Teste da Máquina de Estados de Modo

 


Através desta simulação podemos ver o comportamento da Máquina de Estados de Edição. O trabalho desta máquina de estados é cada vez que um botão é clicado, a variável de saída muda de valor, como podemos confirmar na simulação.

7. Teste do Principal

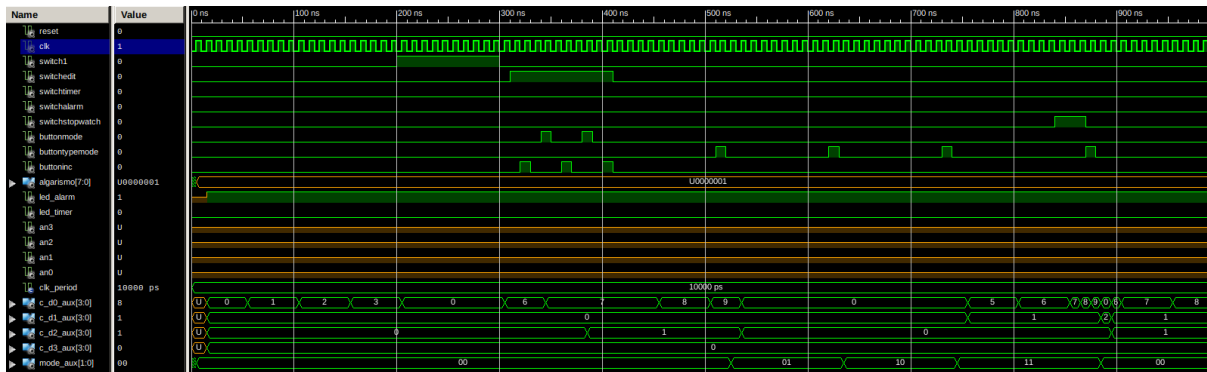

Através desta simulação podemos ver o comportamento do ficheiro principal. Temos as variáveis `c_d0_aux`, `c_d1_aux`, `c_d2_aux` e `c_d3_aux` que correspondem aos dígitos do display. Mexemos com o relógio inicialmente, acertamos as hh:mm:ss, de seguida mudamos para o display do alarme, temporizador, cronómetro e de volta para o relógio.

8. Teste do Debouncer

 

Através desta simulação podemos ver o comportamento do Debouncer.

No real o botão tem uma oscilação e quando estabiliza é que é que envia o pulso a ON. Neste caso para testar, como não houve oscilações passados 10 clocks o pulso foi enviado.

Anexos

1. Relógio

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;

entity relógio is
    Port ( clk : in std_logic;
          reset : in std_logic;

          switchEDIT : in std_logic;
          incSec : in std_logic;
          incMin : in std_logic;
          incHour : in std_logic;

          c_seg_u : out std_logic_vector(3 downto 0);
          c_seg_d : out std_logic_vector(3 downto 0);
          c_min_u : out std_logic_vector(3 downto 0);
          c_min_d : out std_logic_vector(3 downto 0);
          c_hour_u : out std_logic_vector(3 downto 0);
          c_hour_d : out std_logic_vector(3 downto 0);

          seg_u_aux : out std_logic
    );
end relógio;

architecture Behavioral of relógio is

    signal cont_subseg : integer range 0 to 50000000;

    signal cont_seg_u, cont_min_u, cont_hour_u : integer range 0 to 9;
    signal cont_seg_d, cont_min_d, cont_hour_d : integer range 0 to 9;
    signal seg_u, seg_d, min_u, min_d, hour_u, hour_d : std_logic;

begin

    process (clk, reset)
    begin
        if reset = '1' then
            cont_subseg <= 0;
            elsif clk'event and clk = '1' and switchEdit = '0' then
                if cont_subseg = 49999999 then--49999999 --4
                    cont_subseg <= 0;
                else cont_subseg <= cont_subseg + 1;
            end if;
        end if;
    end process;

    seg_u <= '1' when cont_subseg = 49999999 else '0';--49999999 --4
    seg_u_aux <= seg_u;

    process (clk, reset)
    begin
        if reset = '1' then
            cont_seg_u <= 0;

            elsif clk'event and clk = '1' then
                if seg_u = '1' or incSec = '1' then
                    if cont_seg_u = 9 then
                        cont_seg_u <= 0;
                    else cont_seg_u <= cont_seg_u + 1;
                end if;
            end if;
        end process;

        seg_d <= '1' when cont_seg_u = 9 and (seg_u = '1' or incSec = '1') else '0';
        c_seg_u <= std_logic_vector(to_unsigned(cont_seg_u,c_seg_u'length));

        process (clk, reset)
        begin
            if reset = '1' then
                cont_seg_d <= 0;
            elsif clk'event and clk = '1' then
                if seg_d = '1' then
                    if cont_seg_d = 5 then
                        cont_seg_d <= 0;
                    else cont_seg_d <= cont_seg_d + 1;
                end if;
            end if;
        end process;

        min_u <= '1' when cont_seg_d = 5 and seg_d = '1' and incSec = '0' else '0';
        c_seg_d <= std_logic_vector(to_unsigned(cont_seg_d,c_seg_d'length));

        process (clk, reset)
        begin
            if reset = '1' then
                cont_min_u <= 0;

                elsif clk'event and clk = '1' then
                    if min_u = '1' or incMin = '1' then
                        if cont_min_u = 9 then
                            cont_min_u <= 0;
                        else cont_min_u <= cont_min_u + 1;
                    end if;
                end if;
            end if;
        end process;
```

```

end process;

min_d <= '1' when cont_min_u = 9 and (min_u = '1' or incMin = '1') else '0';
c_min_u <= std_logic_vector(to_unsigned(cont_min_u,c_min_u'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_min_d <= 0;
    elsif clk'event and clk = '1' then
        if min_d = '1' then
            if cont_min_d = 5 then
                cont_min_d <= 0;
            else cont_min_d <= cont_min_d + 1;
            end if;
        end if;
    end if;
end process;

hour_u <= '1' when cont_min_d = 5 and min_d = '1' and incMin = '0' else '0';
c_min_d <= std_logic_vector(to_unsigned(cont_min_d,c_min_d'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_hour_u <= 0;

    elsif clk'event and clk = '1' then
        if hour_u = '1' or incHour = '1' then
            if cont_hour_d = 2 and cont_hour_u = 3 then
                cont_hour_u <= 0;

            elsif cont_hour_u = 9 then
                cont_hour_u <= 0;
            else cont_hour_u <= cont_hour_u + 1;
            end if;
        end if;
    end if;
end process;

hour_d <= '1' when (cont_hour_u = 9 or (cont_hour_u = 3 and cont_hour_d = 2)) and (hour_u = '1' or incHour = '1') else '0'; --or (cont_hour_u = 3 and cont_hour_d = 2))
c_hour_u <= std_logic_vector(to_unsigned(cont_hour_u,c_hour_u'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_hour_d <= 0;
    elsif clk'event and clk = '1' then
        if hour_d = '1' then
            if cont_hour_d = 2 and cont_hour_u = 3 then
                cont_hour_d <= 0;
            else cont_hour_d <= cont_hour_d + 1;
            end if;
        end if;
    end if;
end process;

c_hour_d <= std_logic_vector(to_unsigned(cont_hour_d,c_hour_d'length));

end Behavioral;

```

2. Alarm

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Alarm is
    Port (
        clk : in std_logic;

        reset : in std_logic;
        incSecAlarm : in std_logic;
        incMinAlarm : in std_logic;
        incHourAlarm : in std_logic;
        buttonSTOP : in std_logic;
        switchALARM : in std_logic;
        c_seg_u : in std_logic_vector(3 downto 0);
        c_seg_d : in std_logic_vector(3 downto 0);
        c_min_u : in std_logic_vector(3 downto 0);
        c_min_d : in std_logic_vector(3 downto 0);
        c_hour_u : in std_logic_vector(3 downto 0);
        c_hour_d : in std_logic_vector(3 downto 0);
        a_seg_u : out std_logic_vector(3 downto 0);
        a_seg_d : out std_logic_vector(3 downto 0);
        a_min_u : out std_logic_vector(3 downto 0);
        a_min_d : out std_logic_vector(3 downto 0);
        a_hour_u : out std_logic_vector(3 downto 0);
        a_hour_d : out std_logic_vector(3 downto 0);
        alarmsRunning : out std_logic
    );
end Alarm;

architecture Behavioral of Alarm is

```

```

signal cont_seg_u, cont_min_u, cont_hour_u : integer range 0 to 9;
signal cont_seg_d, cont_min_d, cont_hour_d : integer range 0 to 9;
signal c_seg_u_aux, c_seg_d_aux, c_min_u_aux, c_min_d_aux, c_hour_u_aux, c_hour_d_aux : std_logic_vector(3 downto 0);
signal seg_d, min_d, hour_d: std_logic;

begin

----- ALARM IS RUNNING -----
process(clk)
begin
    if clk'event and clk = '1' then
        if (switchALARM = '0') then
            if (std_logic_vector(to_unsigned(cont_seg_u,a_seg_u'length)) = c_seg_u_aux and
            std_logic_vector(to_unsigned(cont_seg_d,a_seg_d'length)) = c_seg_d_aux and
            std_logic_vector(to_unsigned(cont_min_u,a_min_u'length)) = c_min_u_aux and
            std_logic_vector(to_unsigned(cont_min_d,a_min_d'length)) = c_min_d_aux and
            std_logic_vector(to_unsigned(cont_hour_u,a_hour_u'length)) = c_hour_u_aux and
            std_logic_vector(to_unsigned(cont_hour_d,a_hour_d'length)) = c_hour_d_aux) then
                alarmsRunning <= '1';
            elsif ((buttonSTOP = '1') or (std_logic_vector(to_unsigned(cont_seg_u,a_seg_u'length)) = c_seg_u_aux and
            std_logic_vector(to_unsigned(cont_seg_d,a_seg_d'length)) = c_seg_d_aux and
            std_logic_vector(to_unsigned(cont_min_u,a_min_u'length)) = c_min_u_aux and
            std_logic_vector(to_unsigned(cont_min_d,a_min_d'length)) = c_min_d_aux and
            std_logic_vector(to_unsigned(cont_hour_u+1,a_hour_u'length)) = c_hour_u_aux and
            std_logic_vector(to_unsigned(cont_hour_d,a_hour_d'length)) = c_hour_d_aux)) then
                alarmsRunning <= '0';
            end if;
        end if;
    end if;
end process;

----- ALARM EDIT -----
process (clk, reset, incSecAlarm)
begin
    if reset = '1' then
        cont_seg_u <= 0;

    elsif clk'event and clk = '1' then
        if incSecAlarm = '1' then
            if cont_seg_u = 9 then
                cont_seg_u <= 0;
            else cont_seg_u <= cont_seg_u + 1;
            end if;
        end if;
    end if;
end process;

seg_d <= '1' when cont_seg_u = 9 and incSecAlarm = '1' else '0';
a_seg_u <= std_logic_vector(to_unsigned(cont_seg_u,a_seg_u'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_seg_d <= 0;

    elsif clk'event and clk = '1' then
        if seg_d = '1' then
            if cont_seg_d = 5 then
                cont_seg_d <= 0;
            else cont_seg_d <= cont_seg_d + 1;
            end if;
        end if;
    end if;
end process;

a_seg_d <= std_logic_vector(to_unsigned(cont_seg_d,a_seg_d'length));

process (clk, reset, incMinAlarm)
begin
    if reset = '1' then
        cont_min_u <= 0;

    elsif clk'event and clk = '1' then
        if incMinAlarm = '1' then
            if cont_min_u = 9 then
                cont_min_u <= 0;
            else cont_min_u <= cont_min_u + 1;
            end if;
        end if;
    end if;
end process;

min_d <= '1' when cont_min_u = 9 and incMinAlarm = '1' else '0';
a_min_u <= std_logic_vector(to_unsigned(cont_min_u,a_min_u'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_min_d <= 0;

    elsif clk'event and clk = '1' then

```

```

                if min_d = '1' then
                    if cont_min_d = 5 then
                        cont_min_d <= 0;
                    else cont_min_d <= cont_min_d + 1;
                    end if;
                end if;
            end if;
        end process;

a_min_d <= std_logic_vector(to_unsigned(cont_min_d,a_min_d'length));

process (clk, reset, incHourAlarm)
begin
    if reset = '1' then
        cont_hour_u <= 0;

        elsif clk'event and clk = '1' then
            if incHourAlarm = '1' then
                if cont_hour_d = 2 and cont_hour_u = 3 then
                    cont_hour_u <= 0;
                elsif cont_hour_u = 9 then
                    cont_hour_u <= 0;
                else cont_hour_u <= cont_hour_u + 1;
                end if;
            end if;
        end if;
    end process;

hour_d <= '1' when (cont_hour_u = 9 or (cont_hour_u = 3 and cont_hour_d = 2)) and incHourAlarm = '1' else '0'; --or (cont_hour_u = 3 and cont_hour_d = 2)
a_hour_u <= std_logic_vector(to_unsigned(cont_hour_u,a_hour_u'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_hour_d <= 0;

        elsif clk'event and clk = '1' then
            if hour_d = '1' then
                if cont_hour_d = 2 and cont_hour_u = 3 then
                    cont_hour_d <= 0;
                else cont_hour_d <= cont_hour_d + 1;
                end if;
            end if;
        end if;
    end process;

a_hour_d <= std_logic_vector(to_unsigned(cont_hour_d,a_hour_d'length));

process(clk)
begin
    if(clk'event and clk = '1') then
        c_hour_d_aux <= c_hour_d;
        c_hour_u_aux <= c_hour_u;
        c_min_d_aux <= c_min_d;
        c_min_u_aux <= c_min_u;
        c_seg_d_aux <= c_seg_d;
        c_seg_u_aux <= c_seg_u;
    end if;
end process;

end Behavioral;

```

3. Timer

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Timer is
    Port ( clk : in  STD_LOGIC;
          reset : in  STD_LOGIC;

          switchTimer : in std_logic;
          incSecTimer : in std_logic;
          incMinTimer : in std_logic;

          t_seg_u : out std_logic_vector(3 downto 0);
          t_seg_d : out std_logic_vector(3 downto 0);
          t_min_u : out std_logic_vector(3 downto 0);
          t_min_d : out std_logic_vector(3 downto 0);

          seg_u_aux : in std_logic;
          timerFinished : out std_logic
        );
end Timer;

architecture Behavioral of Timer is

    signal cont_seg_u, cont_min_u: integer range 0 to 9;
    signal cont_seg_d, cont_min_d: integer range 0 to 9;
    signal iseg_d, imin_d, dseg_d, dmin_u, dmin_d, timerFinished_aux : std_logic;

```

```

begin

----- RUNNING TIMER -----

process(clk, cont_seg_u, cont_min_u, cont_seg_d, cont_min_d)
begin
    if(cont_seg_u = 0 and cont_seg_d = 0 and cont_min_u = 0 and cont_min_d = 0) then
        timerFinished_aux <= '1';
    else
        timerFinished_aux <= '0';
    end if;
end process;

timerFinished <= timerFinished_aux;

----- EDIT TIMER -----

process (clk, reset)
begin
    if reset = '1' then
        cont_seg_u <= 0;

        elsif clk'event and clk = '1' then
            -- ACERTO DOS SEGUNDOS UNIDADES --
            if incSecTimer = '1' then
                if cont_seg_u = 9 then
                    cont_seg_u <= 0;
                    else cont_seg_u <= cont_seg_u + 1;
                end if;

            -- TIMER A DECREMENTAR --
            elsif seg_u_aux = '1' and timerFinished_aux = '0' and switchTimer = '0' then
                if cont_seg_u = 0 then
                    cont_seg_u <= 9;
                    else cont_seg_u <= cont_seg_u - 1;
                end if;
            end if;
        end if;
end process;

iseg_d <= '1' when cont_seg_u = 9 and incSecTimer = '1' else '0';
dseg_d <= '1' when (cont_seg_u = 0 and timerFinished_aux = '0' and switchTimer = '0' and (cont_seg_d > 0 or cont_min_u > 0 or cont_min_d > 0)) else '0';
t_seg_u <= std_logic_vector(to_unsigned(cont_seg_u,t_seg_u'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_seg_d <= 0;
    elsif clk'event and clk = '1' then
        if iseg_d = '1' then
            if cont_seg_d = 5 then
                cont_seg_d <= 0;
                else cont_seg_d <= cont_seg_d + 1;
            end if;
        elsif seg_u_aux = '1' and dseg_d = '1' then
            if cont_seg_d = 0 then
                cont_seg_d <= 5;
                else cont_seg_d <= cont_seg_d - 1;
            end if;
        end if;
    end if;
end process;

dmin_u <= '1' when ((cont_seg_d = 0 and cont_seg_u = 0) and timerFinished_aux = '0' and switchTimer = '0' and (cont_min_u > 0 or cont_min_d > 0)) else '0';
t_seg_d <= std_logic_vector(to_unsigned(cont_seg_d,t_seg_d'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_min_u <= 0;
    elsif clk'event and clk = '1' then
        if incMinTimer = '1' then
            if cont_min_u = 9 then
                cont_min_u <= 0;
                else cont_min_u <= cont_min_u + 1;
            end if;
        elsif seg_u_aux = '1' and dmin_u = '1' then
            if cont_min_u = 0 then
                cont_min_u <= 9;
                else cont_min_u <= cont_min_u - 1;
            end if;
        end if;
    end if;
end process;

imin_d <= '1' when cont_min_u = 9 and incMinTimer = '1' else '0';
dmin_d <= '1' when ((cont_min_u = 0 and cont_seg_d = 0 and cont_seg_u = 0) and timerFinished_aux = '0' and switchTimer = '0' and cont_min_d > 0) else '0';
t_min_u <= std_logic_vector(to_unsigned(cont_min_u,t_min_u'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_min_d <= 0;
    elsif clk'event and clk = '1' then
        if imin_d = '1' then
            if cont_min_d = 5 then
                cont_min_d <= 0;
                else cont_min_d <= cont_min_d + 1;
            end if;
        elsif seg_u_aux = '1' and dmin_d = '1' then
            if cont_min_d = 0 then
                cont_min_d <= 5;
                else cont_min_d <= cont_min_d - 1;
            end if;
        end if;
    end if;
end process;

```

```

        end if;
    end process;

    t_min_d <= std_logic_vector(to_unsigned(cont_min_d.t_min_d'length));

end Behavioral;

```

4. Stopwatch

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Stopwatch is
    Port ( clk : in  STD_LOGIC;
          reset : in  STD_LOGIC;

          switchStopWatch : in std_logic;

          sw_mseg_u : out std_logic_vector(3 downto 0);
          sw_mseg_d : out std_logic_vector(3 downto 0);
          sw_seg_u : out std_logic_vector(3 downto 0);
          sw_seg_d : out std_logic_vector(3 downto 0));
end Stopwatch;

architecture Behavioral of Stopwatch is

    signal cont_msubseg : integer range 0 to 500000;

    signal cont_mseg_u, cont_seg_u : integer range 0 to 9;
    signal cont_mseg_d, cont_seg_d : integer range 0 to 9;
    signal mseg_u, mseg_d, seg_u, seg_d : std_logic;

begin

    process (clk, reset)
    begin
        if reset = '1' then
            cont_msubseg <= 0;
            elsif clk'event and clk = '1' and switchStopWatch = '0' then
                if cont_msubseg = 4 then--499999 --4
                    cont_msubseg <= 0;
                    else cont_msubseg <= cont_msubseg + 1;
                end if;
            end if;
        end process;

    mseg_u <= '1' when cont_msubseg = 4 else '0';--499999 --4

    process (clk, reset)
    begin
        if reset = '1' then
            cont_mseg_u <= 0;
            elsif clk'event and clk = '1' then
                if mseg_u = '1' then
                    if cont_mseg_u = 9 then
                        cont_mseg_u <= 0;
                    else cont_mseg_u <= cont_mseg_u + 1;
                    end if;
                end if;
            end if;
        end process;

    mseg_d <= '1' when cont_mseg_u = 9 and mseg_u = '1' else '0';
    sw_mseg_u <= std_logic_vector(to_unsigned(cont_mseg_u,sw_mseg_u'length));

    process (clk, reset)
    begin
        if reset = '1' then
            cont_mseg_d <= 0;
            elsif clk'event and clk = '1' then
                if mseg_d = '1' then
                    if cont_mseg_d = 9 then
                        cont_mseg_d <= 0;
                    else cont_mseg_d <= cont_mseg_d + 1;
                    end if;
                end if;
            end if;
        end process;

    seg_u <= '1' when cont_mseg_d = 9 and mseg_d = '1' else '0';
    sw_mseg_d <= std_logic_vector(to_unsigned(cont_mseg_d,sw_mseg_d'length));

    process (clk, reset)
    begin
        if reset = '1' then
            cont_seg_u <= 0;

            elsif clk'event and clk = '1' then
                if seg_u = '1' then
                    if cont_seg_u = 9 then
                        cont_seg_u <= 0;
                    else cont_seg_u <= cont_seg_u + 1;

```

```

        end if;
    end if;
end if;
end process;

seg_d <= '1' when cont_seg_u = 9 and seg_u = '1' else '0';
sw_seg_u <= std_logic_vector(to_unsigned(cont_seg_u,sw_seg_u'length));

process (clk, reset)
begin
    if reset = '1' then
        cont_seg_d <= 0;
    elsif clk'event and clk = '1' then
        if seg_d = '1' then
            if cont_seg_d = 5 then
                cont_seg_d <= 0;
            else cont_seg_d <= cont_seg_d + 1;
            end if;
        end if;
    end if;
end process;

sw_seg_d <= std_logic_vector(to_unsigned(cont_seg_d,sw_seg_d'length));

end Behavioral;

```

5. Conversor do Display

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;

entity conv_displays is
    Port ( clk : in std_logic;
          reset : in std_logic;
          seg_u : in std_logic_vector(3 downto 0);
          seg_d : in std_logic_vector(3 downto 0);
          min_u : in std_logic_vector(3 downto 0);
          min_d : in std_logic_vector(3 downto 0);
          an3 : out std_logic;
          an2 : out std_logic;
          an1 : out std_logic;
          an0 : out std_logic;
          algarismo : out std_logic_vector(7 downto 0));
end conv_displays;

architecture Behavioral of conv_displays is
    signal alg : integer range 0 to 9;
    signal cont_clock : integer range 0 to 499999;
    signal num_alg : std_logic_vector(1 downto 0);

begin

    co: process (clk, reset)
    begin
        if reset = '1' then
            cont_clock <= 0;
        elsif clk'event and clk = '1' then
            if cont_clock = 499999 then
                cont_clock <= 0;
                num_alg <= "00";
            else
                if cont_clock = 124999 then
                    num_alg <= "01";
                elsif cont_clock = 249999 then
                    num_alg <= "10";
                elsif cont_clock = 374999 then
                    num_alg <= "11";
                end if;
                cont_clock <= cont_clock + 1;
            end if;
        end if;
    end process;

    an : process(clk, reset)
    begin
        if reset = '1' then
            an3 <= '0';
            an2 <= '0';
            an1 <= '0';
            an0 <= '0';
            alg <= 0;
            algarismo(7) <= '1';
        elsif clk'event and clk = '1' then
            if num_alg = "00" then
                an3 <= '0';
                an2 <= '1';
                an1 <= '1';
                an0 <= '1';
                alg <= to_integer(unsigned(seg_u));
                algarismo(7) <= '1';
            elsif num_alg = "01" then
                an3 <= '1';
                an2 <= '0';
                an1 <= '1';
                an0 <= '1';
                alg <= to_integer(unsigned(seg_d));
                algarismo(7) <= '1';
            elsif num_alg = "10" then
                an3 <= '1';
                an2 <= '1';
            end if;
        end if;
    end process;
end Behavioral;

```

```

an1 <= '0';
an0 <= '1';
alg <= to_integer(unsigned(min_u));
algarismo(7) <= '0';
elsif num_alg = "11" then
an3 <= '1';
an2 <= '1';
an1 <= '1';
an0 <= '0';
alg <= to_integer(unsigned(min_d));
algarismo(7) <= '1';
end if;
end if;
end process;

al : process(clk, reset)
begin
if reset = '1' then
algarismo(6 downto 0) <= "0000001";
elsif clk'event and clk = '1' then
case alg is
when 0 => algarismo(6 downto 0) <= "0000001";
when 1 => algarismo(6 downto 0) <= "1001111";
when 2 => algarismo(6 downto 0) <= "0010010";
when 3 => algarismo(6 downto 0) <= "0000110";
when 4 => algarismo(6 downto 0) <= "1001100";
when 5 => algarismo(6 downto 0) <= "0100100";
when 6 => algarismo(6 downto 0) <= "0100000";
when 7 => algarismo(6 downto 0) <= "0001111";
when 8 => algarismo(6 downto 0) <= "0000000";
when 9 => algarismo(6 downto 0) <= "0000100";
when others => algarismo(6 downto 0) <= "0111000";
end case;
end if;
end process;

end Behavioral;

```

6. Máquina de Estados do Modo

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Mode_State_Machine is
Port (
clk : in STD_LOGIC ;
buttonTYPEMODE : in STD_LOGIC ;
mode : out STD_LOGIC_VECTOR(1 DOWNTO 0)
);
end Mode_State_Machine;

architecture Behavioral of Mode_State_Machine is
--Use descriptive names for the states, like st1_reset, st2_search
type state_type is (watch, alarm, timer, stopwatch); --
signal state, next_state : state_type;

--Declare internal signals for all outputs of the state-machine
signal mode_i : std_logic_vector(1 downto 0);

--signal mode_aux : integer range 0 to 2;

begin

SYNC_PROC: process (clk)
begin
if (clk'event and clk = '1') then
state <= next_state;

mode_i <= mode_i;
-- assign other outputs to internal signals
end if;
end process;

--MOORE State-Machine - Outputs based on state only
OUTPUT_DECODE: process (state)
begin
--insert statements to decode internal output signals
--below is simple example
if state = watch then
else
end if;
end process;

NEXT_STATE_DECODE: process (state, buttonTYPEMODE)
begin
--declare default state for next_state to avoid latches
next_state <= state; --default is to stay in current state
--insert statements to decode next_state
--below is a simple example
case (state) is
when watch =>
mode_i <= "00";

if buttonTYPEMODE = '1' then

```



```

        next_state <= alarm;
    else
        next_state <= watch;
    end if;
when alarm =>
    if buttonTYPEMODE = '1' then
        next_state <= timer;
    else
        next_state <= alarm;
    end if;
when timer =>
    mode_i <= "10";
    if buttonTYPEMODE = '1' then
        next_state <= stopwatch;
    else
        next_state <= timer;
    end if;
when stopwatch =>
    mode_i <= "11";
    if buttonTYPEMODE = '1' then
        next_state <= watch;
    else
        next_state <= stopwatch;
    end if;
when others =>
    next_state <= watch;
end case;
end process;

end Behavioral;

```

7. Máquina de Estados da Edição

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity State_machine is
--Insert the following in the architecture before the begin keyword
    Port (

```

```

        clk : in std_logic;
        reset : in std_logic;
        switchEDIT : in std_logic;
        switchTIMER : in std_logic;
        switchALARM : in std_logic;
        buttonMODE : in std_logic;
        buttonINC : in std_logic;
        incSec : out std_logic;
        incMin : out std_logic;
        incHour : out std_logic;
        incSecAlarm : out std_logic;
        incMinAlarm : out std_logic;
        incHourAlarm : out std_logic;
        incSecTimer : out std_logic;
        incMinTimer : out std_logic;
    );
end State_machine;

```

```

architecture Behavioral of State_machine is

```

```

--Use descriptive names for the states, like st1_reset, st2_search
type state_type is (
    st0_idle, st1_seconds, st2_minutes, st3_hours, st4_incsec, st5_incmn, st6_inchour,

```

```

    SincHourAlarm,

```

```

    signal state, next_state : state_type;

```

```

--Declare internal signals for all outputs of the state-machine
signal incSec_i : std_logic;
signal incMin_i : std_logic;
signal incHour_i : std_logic;

```

```

    signal incSecAlarm_i : std_logic;
signal incMinAlarm_i : std_logic;
signal incHourAlarm_i : std_logic;

```

```

    signal incSecTimer_i : std_logic;
signal incMinTimer_i : std_logic;

```

```

--other outputs

```

```

begin

```

```

SYNC_PROC: process (clk)
begin

```

```

    if (clk'event and clk = '1') then
        if (reset = '1') then
            state <= st0_idle;
            incSec <= '0';
            incMin <= '0';
            incHour <= '0';

```

```

            incMinAlarm <= '0';

```

```

            incSecAlarm <= '0';

```

```

            secAlarm, minAlarm, hourAlarm, SincSecAlarm, SincMinAlarm,

```

```

            secTimer, minTimer, SincSecTimer, SincMinTimer);

```

```

incHourAlarm <= '0';
incMinTimer <= '0';
else
state <= next_state;
incSec <= incSec_i;
incMin <= incMin_i;
incHour <= incHour_i;
incMinAlarm <= incMinAlarm_i;
incHourAlarm <= incHourAlarm_i;
incMinTimer <= incMinTimer_i;
-- assign other outputs to internal signals
end if;
end if;
end process;

--MOORE State-Machine - Outputs based on state only
OUTPUT_DECODE: process (state)
begin
--insert statements to decode internal output signals
--below is simple example
if state = st3_hours then
else
end if;
end process;

NEXT_STATE_DECODE: process (state, buttonMODE, switchEDIT, switchALARM, switchTIMER, buttonINC)
begin
--declare default state for next_state to avoid latches
next_state <= state;
case (state) is
when st0_idle =>
if switchEDIT = '1' then
next_state <= st1_seconds;
elsif switchALARM = '1' then
next_state <= secAlarm;
elsif switchTIMER = '1' then
next_state <= secTimer;
else
next_state <= st0_idle;
end if;

-- WATCH STATE MACHINE PART --
when st1_seconds =>
if switchEDIT = '0' then
next_state <= st0_idle;
elsif buttonINC = '1' then
next_state <= st4_incsec;
else
next_state <= st1_seconds;
end if;

when st2_minutes =>
if switchEDIT = '0' then
next_state <= st0_idle;
elsif buttonINC = '1' then
next_state <= st5_incmin;
else
next_state <= st2_minutes;
end if;

when st3_hours =>
if switchEDIT = '0' then
next_state <= st0_idle;
elsif buttonINC = '1' then
next_state <= st6_inchour;
else
next_state <= st3_hours;
end if;

when st4_incsec =>
if buttonINC = '0' then
next_state <= st1_seconds;
else
next_state <= st4_incsec;
end if;

when st5_incmin =>
if buttonINC = '0' then
next_state <= st2_minutes;
else
next_state <= st5_incmin;
end if;

when st6_inchour =>
if buttonINC = '0' then
next_state <= st3_hours;
else
next_state <= st6_inchour;
end if;

-- ALARM STATE MACHINE PART --
when secAlarm =>
if switchALARM = '0' then
next_state <= st0_idle;
elsif buttonINC = '1' then
next_state <= SincSecAlarm;

```

```

elseif buttonMODE = '1' then
    next_state <= minAlarm;
    else
    next_state <=secAlarm;
    end if;

when minAlarm =>
    if switchALARM = '0' then
        next_state <= st0_idle;
    elseif buttonINC = '1' then
        next_state <= SincMinAlarm;
    elseif buttonMODE = '1' then
        next_state <= hourAlarm;
        else
        next_state <=minAlarm;
        end if;

when hourAlarm =>
    if switchALARM = '0' then
        next_state <= st0_idle;
    elseif buttonINC = '1' then
        next_state <= SincHourAlarm;
    elseif buttonMODE = '1' then
        next_state <= secAlarm;
        else
        next_state <=hourAlarm;
        end if;

when SincSecAlarm =>
    if buttonINC = '0' then
        next_state <= secAlarm;
        else
        next_state <=SincSecAlarm;
        end if;

when SincMinAlarm =>
    if buttonINC = '0' then
        next_state <= minAlarm;
        else
        next_state <=SincMinAlarm;
        end if;

when SincHourAlarm =>
    if buttonINC = '0' then
        next_state <= hourAlarm;
        else
        next_state <=SincHourAlarm;
        end if;

-- TIMER STATE MACHINE PART --

when secTimer =>
    if switchTIMER = '0' then
        next_state <= st0_idle;
    elseif buttonINC = '1' then
        next_state <= SincSecTimer;
    elseif buttonMODE = '1' then
        next_state <= minTimer;
    else
    next_state <=secTimer;
    end if;

when minTimer =>
    if switchTIMER = '0' then
        next_state <= st0_idle;
    elseif buttonINC = '1' then
        next_state <= SincMinTimer;
    elseif buttonMODE = '1' then
        next_state <= secTimer;
    else
    next_state <= minTimer;
    end if;

when SincSecTimer =>
    if buttonINC = '0' then
        next_state <= secTimer;
    else
    next_state <= SincSecTimer;
    end if;

when SincMinTimer =>
    if buttonINC = '0' then
        next_state <= minTimer;
    else
    next_state <=SincMinTimer;
    end if;

when others =>
    next_state <= st0_idle;
end case;
end process;

incSec_j <= '1' when (state = st1_seconds and buttonINC = '1') else '0';
incMin_j <= '1' when (state = st2_minutes and buttonINC = '1') else '0';
incHour_i <= '1' when (state = st3_hours and buttonINC = '1') else '0';

incSecAlarm_j <= '1' when (state = secAlarm and buttonINC = '1') else '0';
incMinAlarm_j <= '1' when (state = minAlarm and buttonINC = '1') else '0';
incHourAlarm_i <= '1' when (state = hourAlarm and buttonINC = '1') else '0';

incSecTimer_j <= '1' when (state = secTimer and buttonINC = '1') else '0';
incMinTimer_j <= '1' when (state = minTimer and buttonINC = '1') else '0';

end Behavioral;

```

8. Debouncer

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Debouncer is
    Port (      clk : in  STD_LOGIC;

                                buttonIn : in STD_LOGIC;
                                buttonOut : out STD_LOGIC

    );
end Debouncer;

architecture Behavioral of Debouncer is

    signal lastButtonState : std_logic := '0';
    signal buttonState : std_logic := '0';
    signal counter : integer range 0 to 10000 := 0;

begin

    process(clk)
    begin
        if(clk'event and clk = '1') then

                                if(buttonIn = '1') then --assuming active-high
                                    if counter < 10000 then
                                        counter <= counter + 1;
                                    else
                                        buttonState <= '1';
                                    end if;
                                else
                                    if counter > 0 then
                                        counter <= counter - 1;
                                    else
                                        buttonState <= '0';
                                    end if;
                                end if;
                            end if;
                        end process;

                    process(clk)
                    begin
                        if(clk'event and clk = '1') then
                            if buttonState = '1' and lastButtonState = '0' then
                                buttonOut <= '1';
                            else
                                buttonOut <= '0';
                            end if;
                            lastButtonState <= buttonState;
                        end if;
                    end process;

                end Behavioral;
```